

# Lab Task\_01

## Implement the 3-to-8 decoder


### VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dec3to8 is
    port (
        input  : in std_logic_vector(2 downto 0);
        output : out std_logic_vector(7 downto 0)
    );
end dec3to8;


architecture Behavioral of dec3to8 is
begin
    output <= "00000001" when (input = "000") else
    "00000010" when (input = "001") else
    "00000100" when (input = "010") else
    "00001000" when (input = "011") else
    "00010000" when (input = "100") else
    "00100000" when (input = "101") else
    "01000000" when (input = "110") else
    "10000000";
end Behavioral;
```

### Simulation:

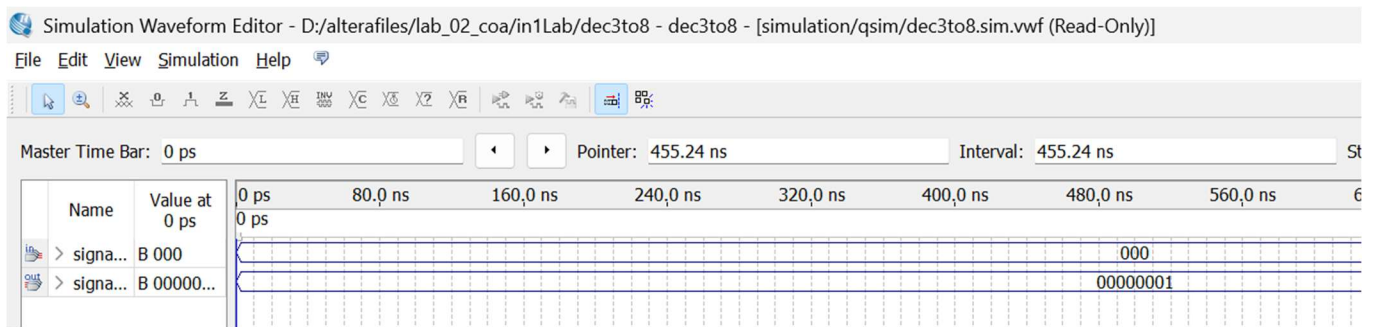

**Simulation 1:** Input is 000, so the respective output is 00000001

## Implementation FPGA Board:

 

*FPGA Hardware 1: All the three inputs are off (0) so only the first output Led is on (1)*

# Lab Task\_02

## Seven Segment Display (SSD)


**VHDL Code:**

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY seven_seg IS
    PORT (
        bininput : IN std_logic_vector(3 DOWNTO 0);
        cathodes : OUT std_logic_vector(6 DOWNTO 0)
    );
END seven_seg;

architecture dataflow of seven_seg is
begin
    cathodes <= "1000000" when (bininput = "0000") else
        "1111001" when (bininput = "0001") else
        "0100100" when (bininput = "0010") else
        "0110000" when (bininput = "0011") else
        "0011001" when (bininput = "0100") else
        "0010010" when (bininput = "0101") else
        "0000010" when (bininput = "0110") else
        "1111000" when (bininput = "0111") else
        "0000000" when (bininput = "1000") else
        "0010000" when (bininput = "1001") else
        "0001000" when (bininput = "1010") else
        "0000011" when (bininput = "1011") else
        "1000110" when (bininput = "1100") else
        "0100001" when (bininput = "1101") else
        "0000110" when (bininput = "1110") else
        "0001110" when (bininput = "1111") else
        "1111111";
end dataflow;
```

## Simulation:

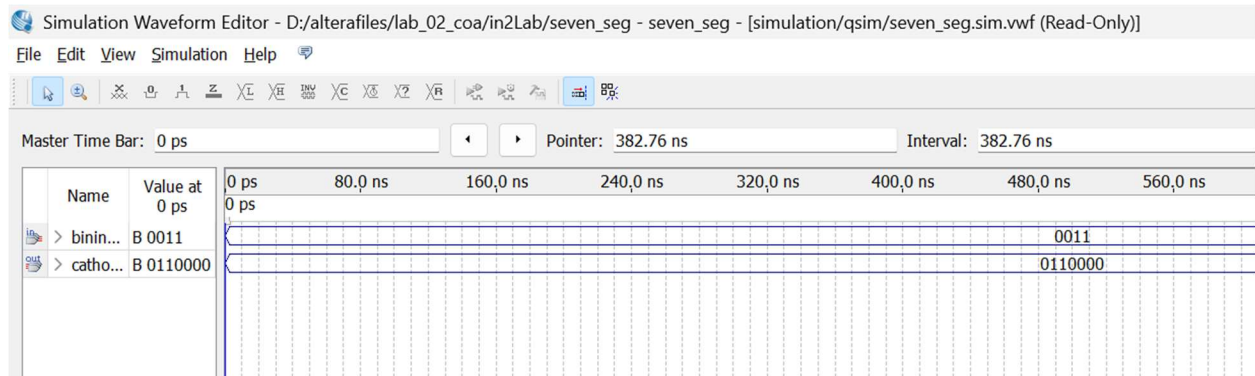

*Simulation 2: Input is 0011, so the respective output is 0110000 which display 3 on seven segment*

## Implementation FPGA Board:



*FPGA Hardware 2: First two input pins are on, so input is 0011, which corresponds to 3 at seven segment display*



*FPGA Hardware 3: First four input pins are on, so input is 1111, which corresponds to F at seven segment display*